

Digital Logic Design

Lecture 11

Don't Care Conditions

- The minterms of a Boolean function specify all combinations of variable values for which the function is equal to 1. The function is assumed to be equal to 0 for the rest of the minterms.
- This assumption, however, is not always valid, since there are applications in which the function is not specified for certain variable value combinations.
- There are two cases in which this occurs.
 - In the first case, the input combinations never occur. As an example, the four-bit binary code for the decimal digits has six combinations that are not used and not expected to occur.
 - In the second case, the input combinations are expected to occur, but we do not care what the outputs are in response to these combinations.

Contd.

- In both cases, the outputs are said to be unspecified for the input combinations.

Incompletely specified functions

- Functions that have unspecified outputs for some input combinations are called incompletely specified functions.
- In most applications, we simply do not care what value is assumed by the function for the unspecified minterms. For this reason, it is customary to call the unspecified minterms of a function don't-care conditions.
- These conditions can be used on a map to provide further simplification of the function.

Contd.

- It should be realized that a don't-care minterm cannot be marked with a 1 on the map, because that would require that the function always be a 1 for such a minterm.
- Likewise, putting a 0 in the square requires the function to be 0.
- To distinguish the don't-care condition from 1s and 0s, an **X** is used.

Simplification of an incompletely specified function

- When choosing adjacent squares to simplify the function in the map, the ×'s may be assumed to be either 0 or 1, whichever gives the simplest expression.
- An × need not be used at all if it does not contribute to covering a larger area.

Example 2.14

- Simplify the Boolean function $F(A, B, C, D) = \sum m(1, 3, 7, 11, 15)$
- which has the don't-care conditions $d(A, B, C, D) = \sum m(0, 2, 5)$.

SOP: $F = CD + \bar{A}\bar{B}$, $F = CD + \bar{A}D$

- It is also possible to obtain an optimized **product-of-sums** expression for the function.

POS: In this case, the way to combine the 0s is to include don't-care minterms 0 and 2 with the 0s, giving the optimized complemented function.

$$\bar{F} = \bar{D} + A\bar{C}$$

Taking the complement of F

$$F = D(\bar{A} + C)$$

		C			
		CD			
A	AB	00	01	11	10
		00	01	11	10
	00	X	1	1	X
	01	0	X	1	0
	11	0	0	1	0
	10	0	0	1	0
		D			

(a) $F = CD + \bar{A}\bar{B}$

		C			
		CD			
A	AB	00	01	11	10
		00	01	11	10
	00	X	1	1	X
	01	0	X	1	0
	11	0	0	1	0
	10	0	0	1	0
		D			

(b) $F = CD + \bar{A}D$

Exclusive OR/ Exclusive NOR

- The *eXclusive OR (XOR)* function is an important Boolean function used extensively in logic circuits.
- The XOR function may be;
 - implemented directly as an electronic circuit (truly a gate) or
 - implemented by interconnecting other gate types (used as a convenient representation)
- The *eXclusive NOR* function is the complement of the XOR function
- By our definition, XOR and XNOR gates are complex gates.

Exclusive OR/ Exclusive NOR

- Uses for the XOR and XNORs gate include:

- Adders/subtractors/multipliers
- Counters/incrementers/decrementers
- Parity generators/checkers

- Definitions

- The XOR function is:
$$X \oplus Y = X \bar{Y} + \bar{X} Y$$

- The eXclusive NOR (XNOR) function, otherwise known as *equivalence* is:
$$\overline{X \oplus Y} = X Y + \bar{X} \bar{Y}$$

- Strictly speaking, XOR and XNOR gates do not exist for more than two inputs. Instead, they are replaced by odd and even functions.

Truth Tables for XOR/XNOR

- Operator Rules: XOR

X	Y	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

- XNOR

X	Y	$\overline{(X \oplus Y)}$ or $X \equiv Y$
0	0	1
0	1	0
1	0	0
1	1	1

- The XOR function means:

X OR Y, but NOT BOTH

- Why is the XNOR function also known as the *equivalence* function, denoted by the operator \equiv ?

XOR/XNOR (Continued)

- The XOR function can be extended to 3 or more variables. For more than 2 variables, it is called an *odd function* or *modulo 2 sum (Mod 2 sum)*, not an XOR:

$$X \oplus Y \oplus Z = \overline{X} \overline{Y} Z + \overline{X} Y \overline{Z} + X \overline{Y} \overline{Z} + X Y Z$$

- The complement of the odd function is the even function.
- The XOR identities:

$$X \oplus 0 = X$$

$$X \oplus X = 0$$

$$X \oplus Y = Y \oplus X$$


$$(X \oplus Y) \oplus Z = X \oplus (Y \oplus Z) = X \oplus Y \oplus Z$$

$$X \oplus 1 = \overline{X}$$


$$X \oplus \overline{X} = 1$$

Symbols For XOR and XNOR

- **XOR symbol:**

 


- **XNOR symbol:**

 


- **Shaped symbols exist only for two inputs**

XOR Implementations

 - The simple SOP implementation uses the following structure:



- A NAND only implementation is:

 


Odd and Even Functions

- The odd and even functions on a K-map form “checkerboard” patterns.
- The 1s of an odd function correspond to minterms having an index with an odd number of 1s.
- The 1s of an even function correspond to minterms having an index with an even number of 1s.
- Implementation of odd and even functions for greater than four variables as a two-level circuit is difficult, so we use “trees” made up of :
 - 2-input XOR or XNORs
 - 3- or 4-input odd or even functions

 
Example: Odd Function Implementation

- Design a 3-input odd function $F = X \oplus Y \oplus Z$ with 2-input XOR gates
- Factoring, $F = (X \oplus Y) \oplus Z$
- The circuit:



 
Example: Even Function Implementation

- Design a 4-input odd function $F = W \oplus X \oplus Y \oplus Z$ with 2-input XOR and XNOR gates
- Factoring, $F = (W \oplus X) \oplus (Y \oplus Z)$
- The circuit:



Parity Generators/ Checkers

- In Chapter 1, a parity bit added to n-bit code to produce an $n + 1$ bit code:
 - Add odd parity bit to generate code words with even parity
 - Add even parity bit to generate code words with odd parity
 - Use odd parity circuit to check code words with even parity
 - Use even parity circuit to check code words with odd parity
- Example: $n = 3$. Generate even parity code words of length four with odd parity generator:
- Check even parity code words of length four with odd parity checker:
- Operation: $(X,Y,Z) = (0,0,1)$ gives $(X,Y,Z,P) = (0,0,1,1)$ and $E = 0$. If Y changes from 0 to 1 between generator and checker, then $E = 1$ indicates an error.

 

Implementing functions with only OR and NOT gates

- $F = \overline{\overline{AB'C} + \overline{A'C'} + \overline{AB}}$

- $F = \overline{\overline{AB'C} + \overline{A'C'} + \overline{AB}}$

- $F = \overline{\overline{AB'C} + \overline{A'C'} + \overline{AB}}$

- By De Morgan's Laws

- $F = \overline{(A' + B + C') \cdot (A + C) \cdot (A' + B')}$

- $F = \overline{(A' + B + C')} + \overline{(A + C)} + \overline{(A' + B')}$

Implementing functions with only AND and NOT gates

- $F = (A+B'+C) \cdot (A'+B+C) \cdot (A'+C) \cdot (B+C')$
- $F = \overline{(A+B'+C) \cdot (A'+B+C) \cdot (A'+C) \cdot (B+C')}$
- $F = \overline{(A+B'+C) + (A'+B+C) + (A'+C) + (B+C')}$
- $F = \overline{(A' \cdot B \cdot C') + (A \cdot B' \cdot C') + (A \cdot C') + (B' \cdot C)}$
- $F = \overline{(A' \cdot B \cdot C') \cdot (A \cdot B' \cdot C') \cdot (A \cdot C') \cdot (B' \cdot C)}$