

Digital Logic Design

Lecture 16

Multiplexing/ De-Multiplexing

Selecting

- **Selecting of data or information is a critical function in digital systems and computers**
- **Circuits that perform selecting have:**
 - ⑩ **A set of information inputs from which the selection is made**
 - ⑩ **A single output**
 - ⑩ **A set of control lines for making the selection**
- **Logic circuits that perform selecting are called *multiplexers***
- **Selecting can also be done by three-state logic or transmission gates**

Multiplexers

- A multiplexer selects information from an input line and directs the information to an output line
- A typical multiplexer has n control inputs (S_{n-1}, \dots, S_0) called *selection inputs*, 2^n information inputs (I_{2^n-1}, \dots, I_0), and one output Y
- A multiplexer can be designed to have m information inputs with $m < 2^n$ as well as n selection inputs


2-to-1-Line Multiplexer

- Since $2 = 2^1$, $n = 1$
- The single selection variable S has two values:
 - ⑩ $S = 0$ selects input I_0
 - ⑩ $S = 1$ selects input I_1

- The equation:

$$Y = \bar{S}I_0 + SI_1$$

- The circuit:

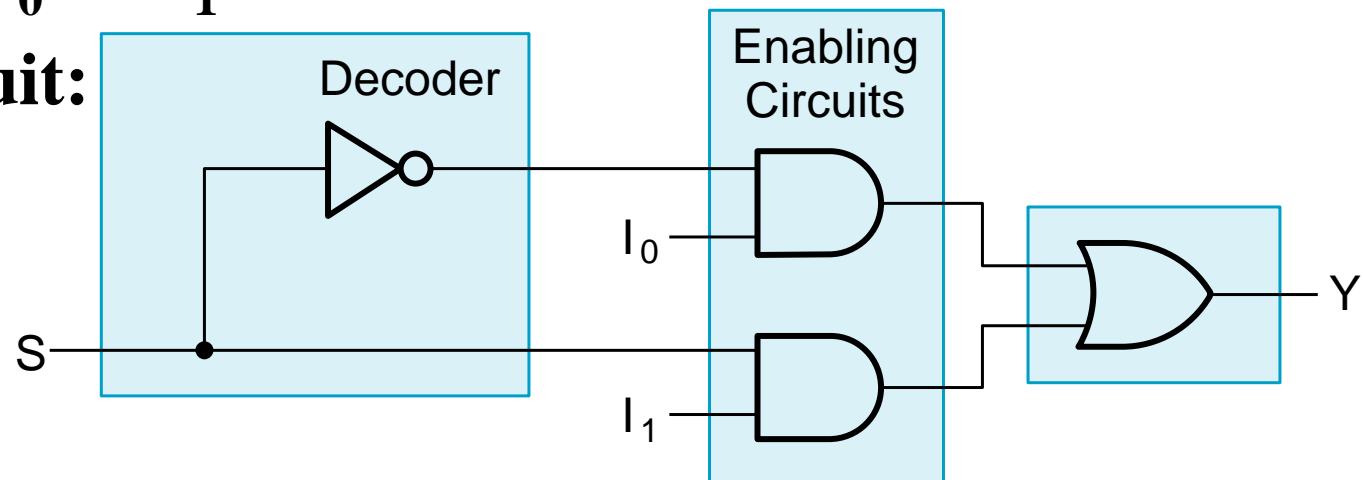


2-to-1-Line Multiplexer (continued)


- **Note the regions of the multiplexer circuit shown:**
 - ⑩ 1-to-2-line Decoder
 - ⑩ 2 Enabling circuits
 - ⑩ 2-input OR gate
- **To obtain a basis for multiplexer expansion, we combine the Enabling circuits and OR gate into a 2×2 AND-OR circuit:**
 - ⑩ 1-to-2-line decoder
 - ⑩ 2×2 AND-OR
- **In general, for an 2^n -to-1-line multiplexer:**
 - ⑩ n -to- 2^n -line decoder
 - ⑩ $2^n \times 2$ AND-OR

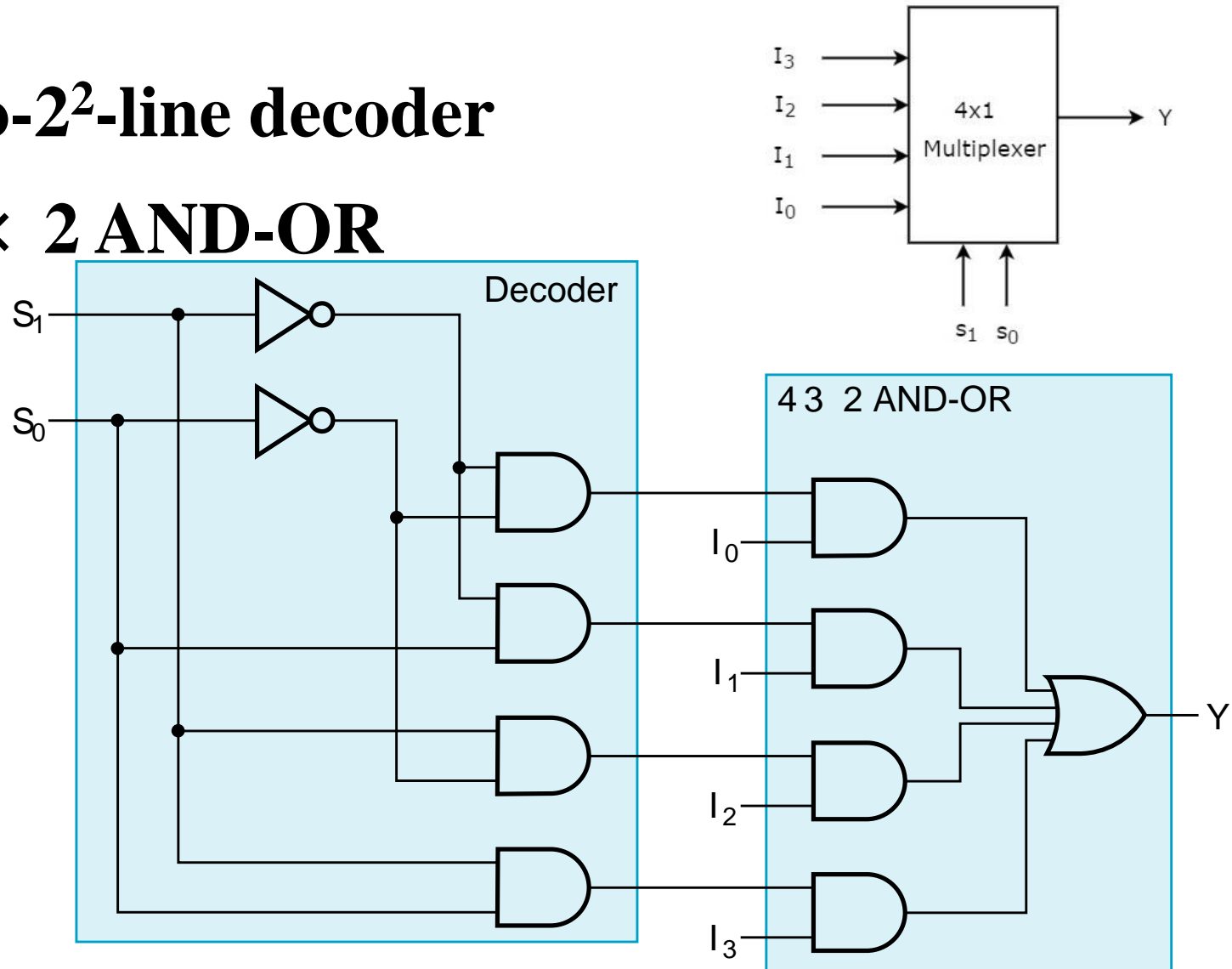Example: 4-to-1-line Multiplexer

- 2-to- 2^2 -line decoder
- $2^2 \times 2$ AND-OR




Example: 8-to-1-line Multiplexer

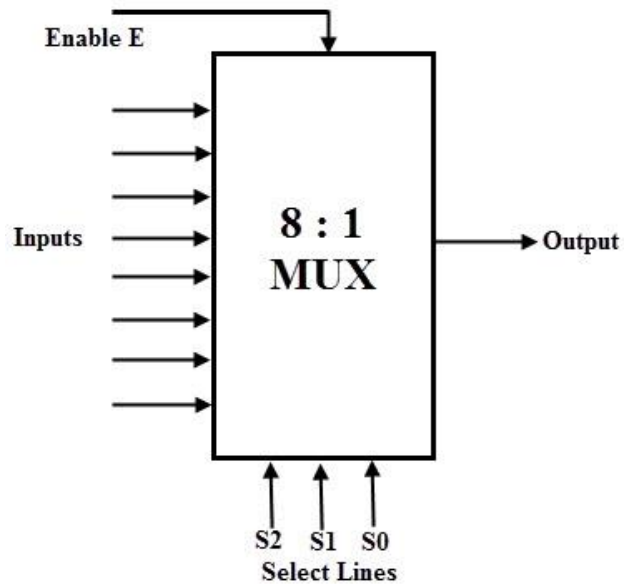


Select Data Inputs			Output
S ₂	S ₁	S ₀	Y
0	0	0	D ₀
0	0	1	D ₁
0	1	0	D ₂
0	1	1	D ₃
1	0	0	D ₄
1	0	1	D ₅
1	1	0	D ₆
1	1	1	D ₇

Example: 8-to-1-line Multiplexer

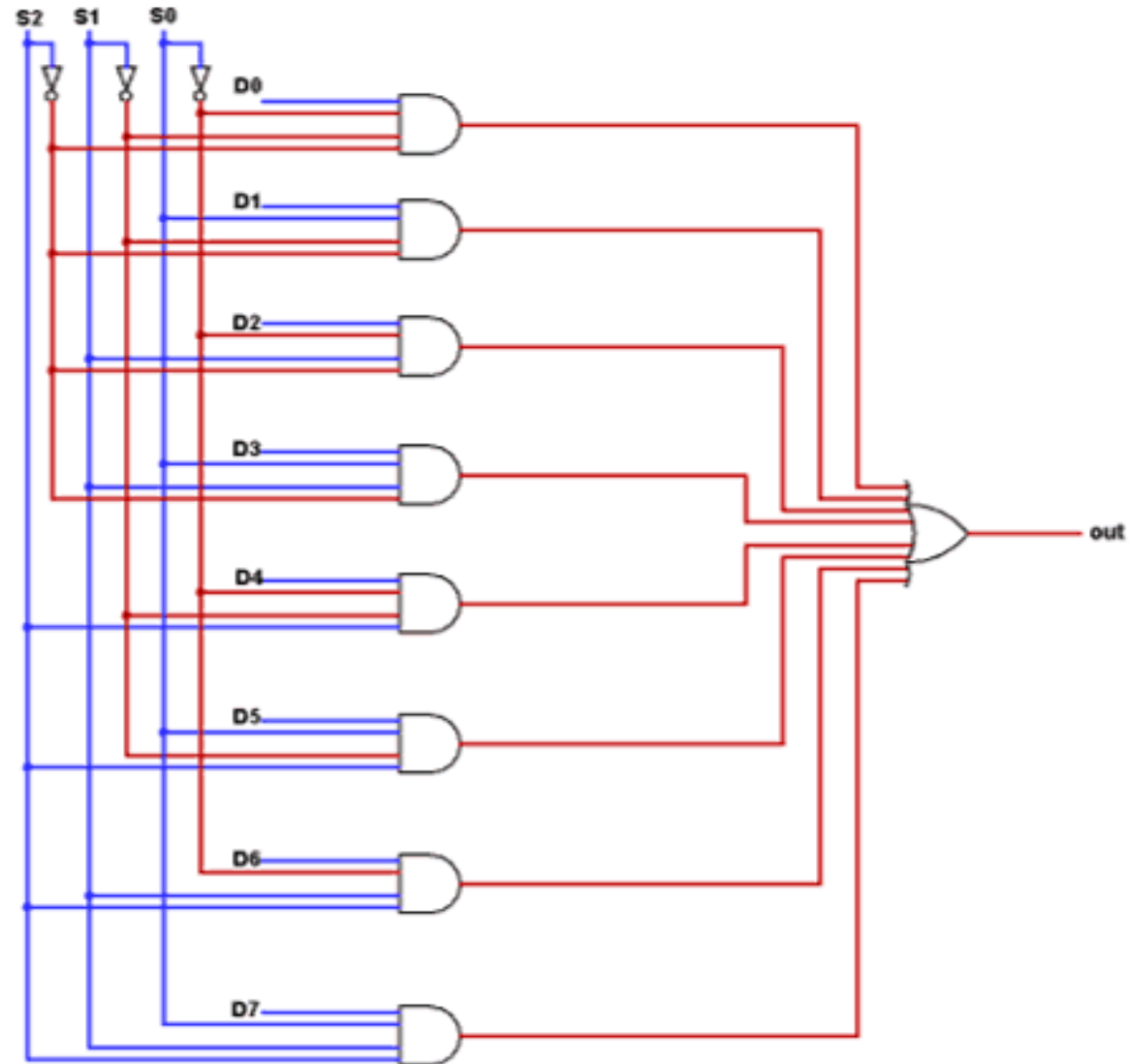

Multiplexer Expansion

- 8-to-1 MUX using Dual 4-to-1 MUX

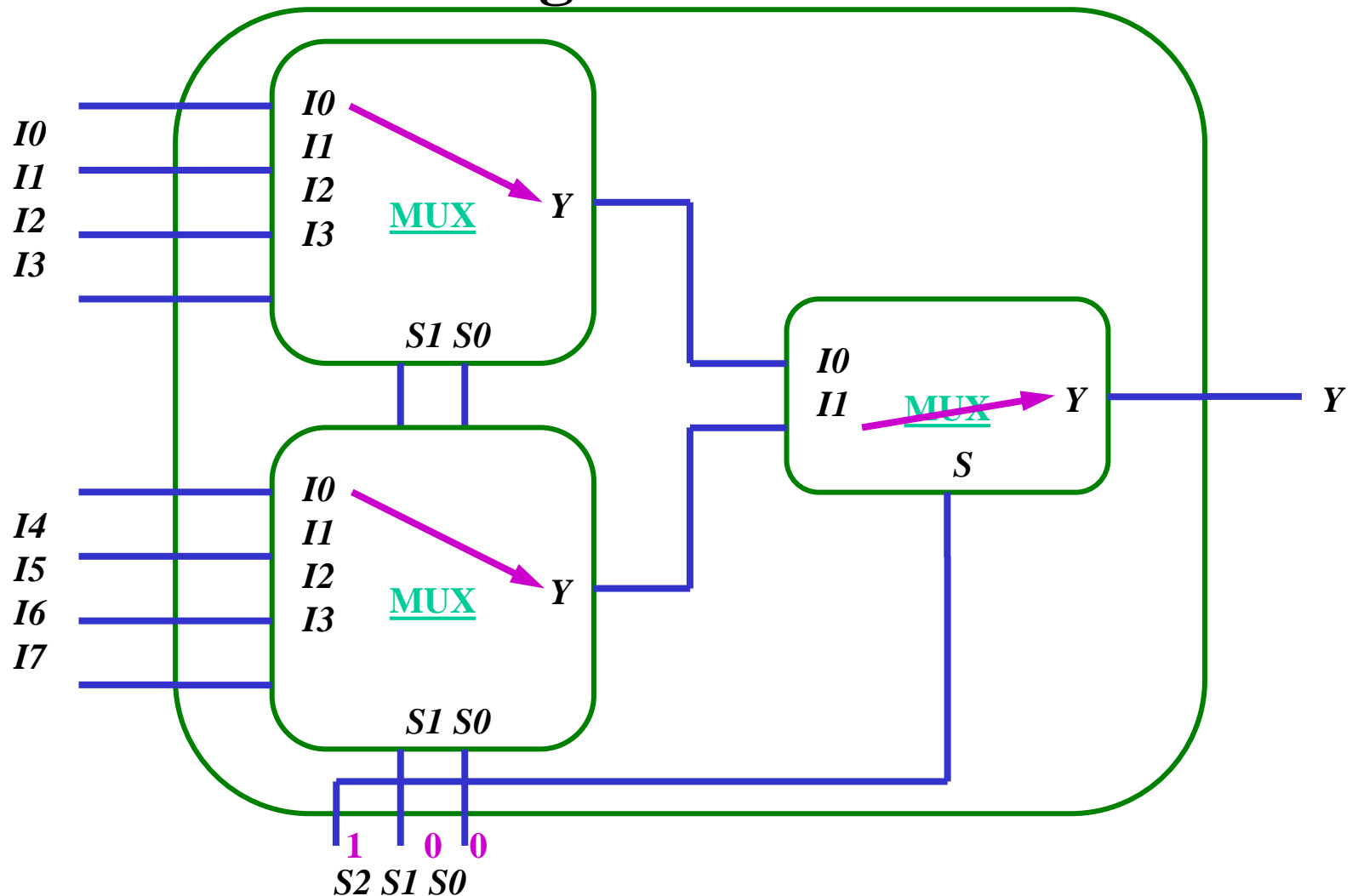

Multiplexer Width Expansion

- Select “vectors of bits” instead of “bits”
- Use multiple copies of $2^n \times 2$ AND-OR in parallel
- Example:
4-to-1-line quad multi-plexer

