

Digital Logic Design

Lecture 14


Decoding

- Decoding - the conversion of an n -bit input code to an m -bit output code with $n \leq m \leq 2^n$ such that each valid code word produces a unique output code
- Circuits that perform decoding are called *decoders*
- Here, functional blocks for decoding are
 - ⑩ called n -to- m line decoders, where $m \leq 2^n$, and
 - ⑩ generate 2^n (or fewer) minterms for the n input variables

Decoder Examples

1-to-2-Line Decoder


A	D_0	D_1
0	1	0
1	0	1

 

2-to-4-Line Decoder

A_1	A_0	D_0	D_1	D_2	D_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

(a)

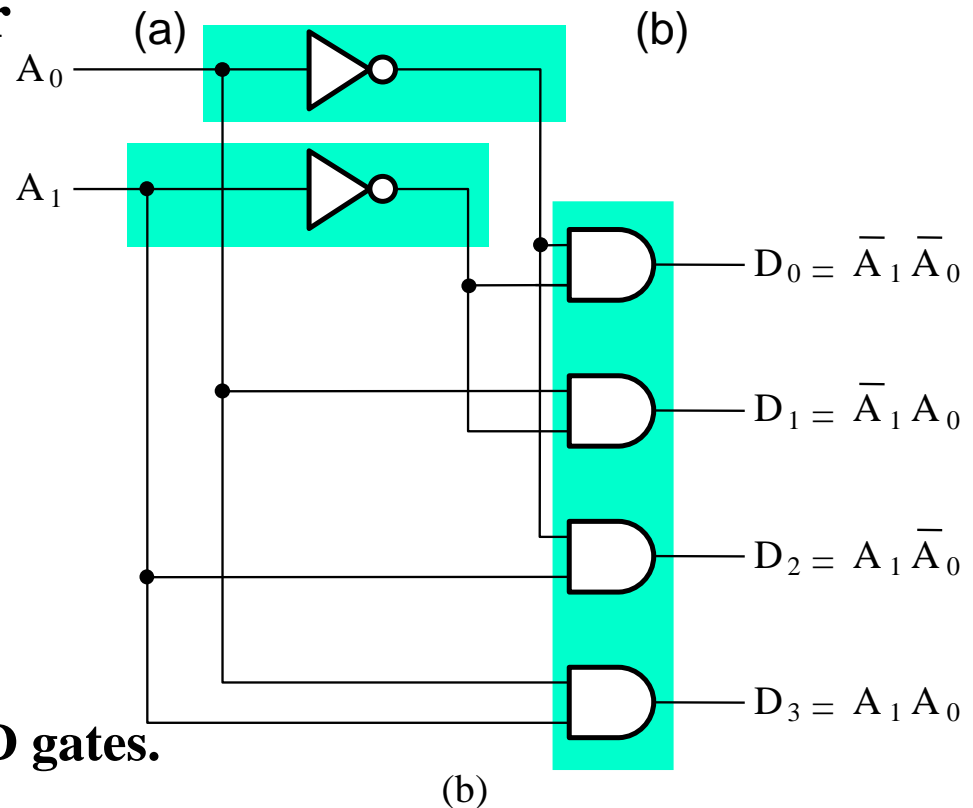

- Note that the 2-4-line made up of 2 1-to-2-line decoders and 4 AND gates.

Decoder Expansion

- General procedure given in book for any decoder with n inputs and 2^n outputs.
- This procedure builds a decoder backward from the outputs.
- The output AND gates are driven by two decoders with their numbers of inputs either equal or differing by 1.
- These decoders are then designed using the same procedure until 2-to-1-line decoders are reached.
- The procedure can be modified to apply to decoders with the number of outputs $\neq 2^n$

Decoder Expansion - Example 1

- 3-to-8-line decoder

- ⑩ Number of output ANDs = 8

- ⑩ Number of inputs to decoders driving output ANDs = 3

- ⑩ Closest possible split to equal

- 2-to-4-line decoder

- 1-to-2-line decoder

- ⑩ 2-to-4-line decoder

- Number of output ANDs = 4

- Number of inputs to decoders driving output ANDs = 2


- Closest possible split to equal

- ⑩ Two 1-to-2-line decoders

- See next slide for result

Decoder Expansion - Example 1

■ Result

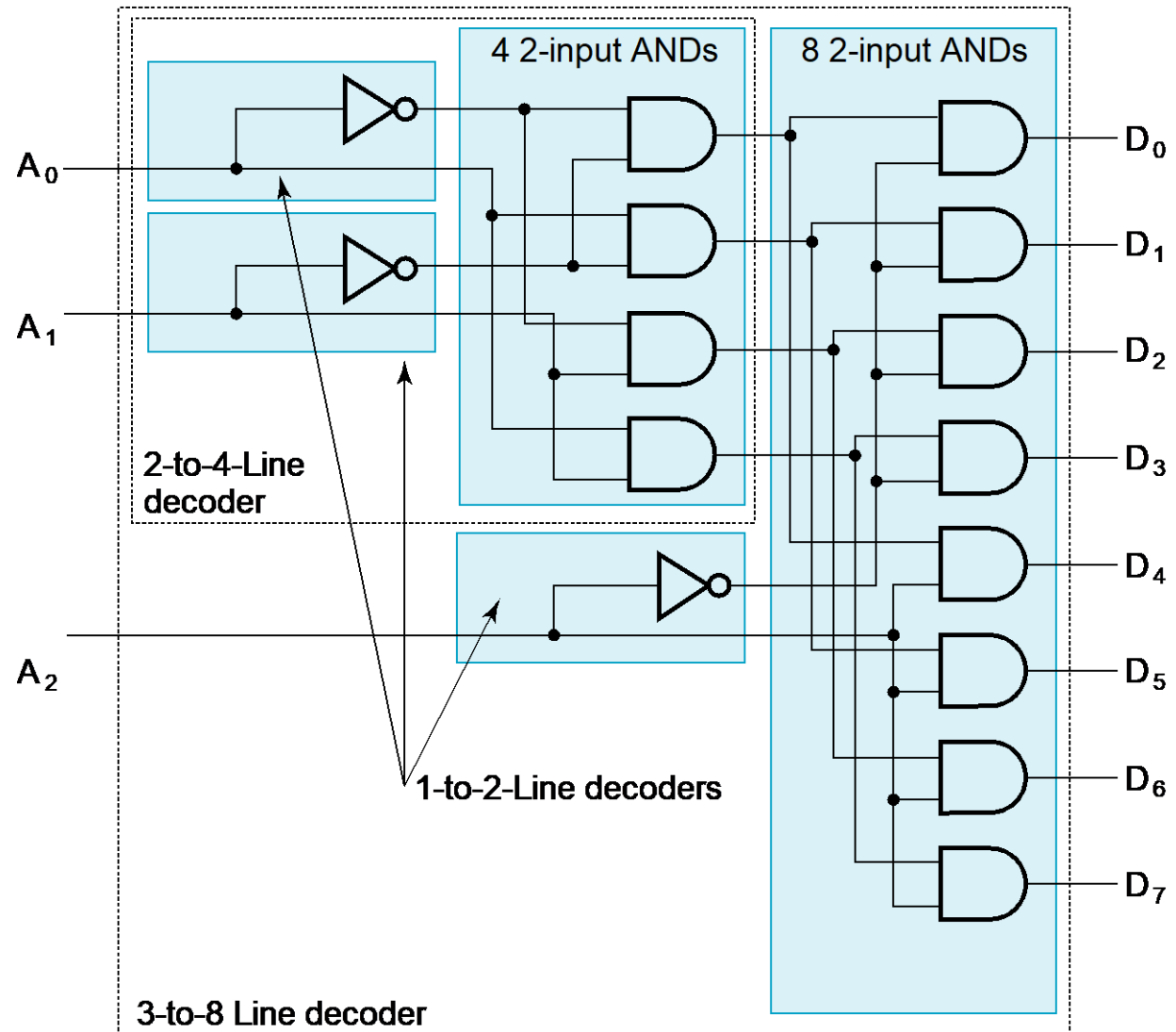

Decoder Expansion - Example 2

- **7-to-128-line decoder**

- ⑩ **Number of output ANDs = 128**

- ⑩ **Number of inputs to decoders driving output ANDs = 7**

- ⑩ **Closest possible split to equal**

- **4-to-16-line decoder**

- **3-to-8-line decoder**

- ⑩ **4-to-16-line decoder**

- **Number of output ANDs = 16**

- **Number of inputs to decoders driving output ANDs = 2**

- **Closest possible split to equal**

- ⑩ **2 2-to-4-line decoders**


- ⑩ **Complete using known 3-8 and 2-to-4 line decoders**

Decoder with Enable

- In general, attach m -enabling circuits to the outputs
- See truth table below for function
 - ⑩ Note use of X's to denote both 0 and 1
 - ⑩ Combination containing two X's represent four binary combinations
- Alternatively, can be viewed as distributing value of signal EN to 1 of 4 outputs
- In this case, called a *demultiplexer*


EN	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

(a)

 

(b)

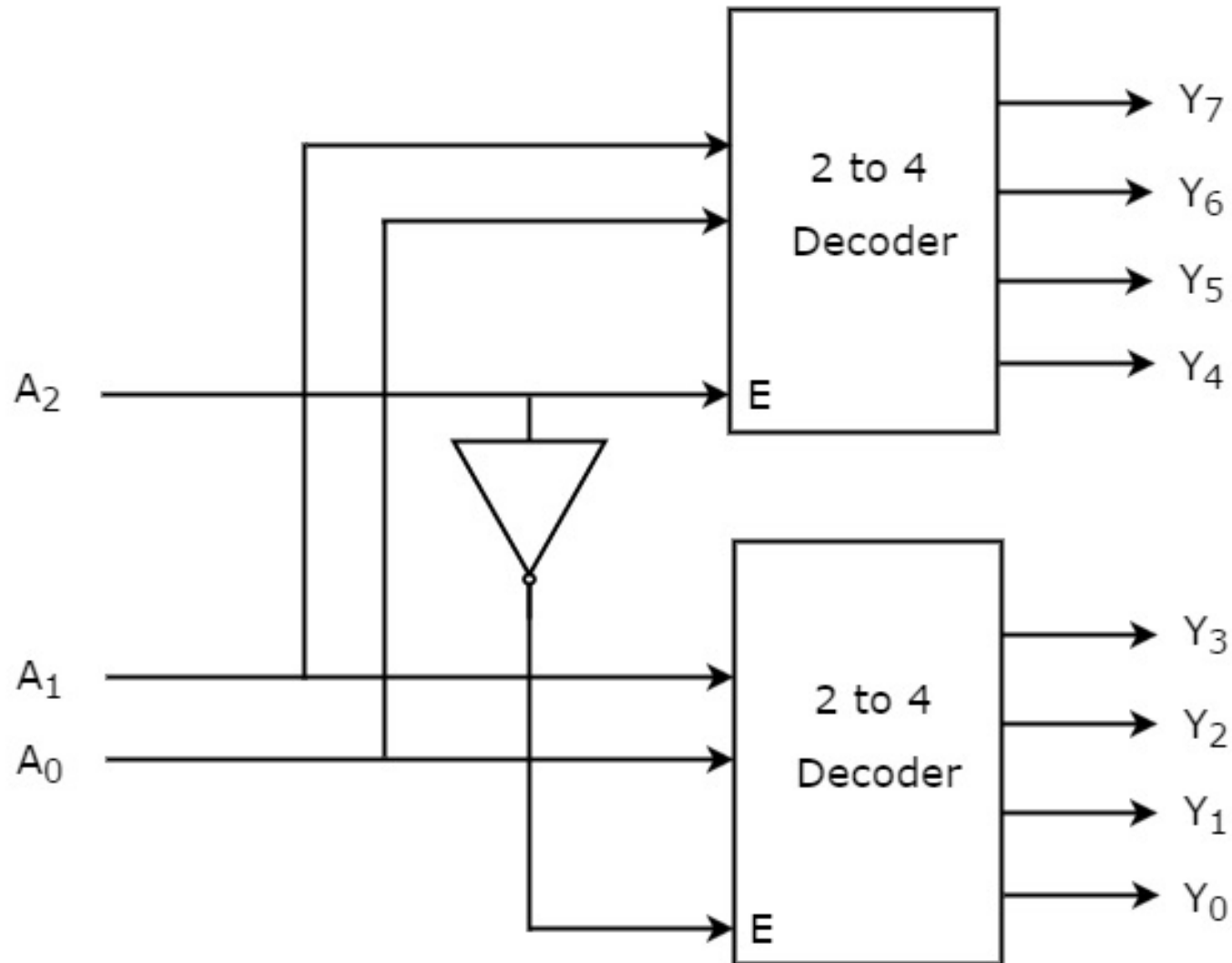3 to 8 line decoder using 2 to 4 line decoder(s)



3 to 8 line decoder using 2 to 4 line decoder(s)

- The parallel inputs A_1 & A_0 are applied to each 2 to 4 decoder.
- The complement of input A_2 is connected to Enable, E of lower 2 to 4 decoder in order to get the outputs, Y_3 to Y_0 . These are the **lower four min terms**.
- The input, A_2 is directly connected to Enable, E of upper 2 to 4 decoder in order to get the outputs, Y_7 to Y_4 . These are the **higher four min terms**.

4 to 16 decoder using 3 to 8 decoders

