

Digital Logic Design

Lecture 17

Selecting

- **Selecting of data or information is a critical function in digital systems and computers**
- **Circuits that perform selecting have:**
 - ⑩ **A set of information inputs from which the selection is made**
 - ⑩ **A single output**
 - ⑩ **A set of control lines for making the selection**
- **Logic circuits that perform selecting are called *multiplexers***
- **Selecting can also be done by three-state logic or transmission gates**

Multiplexers

- A multiplexer selects information from an input line and directs the information to an output line
- A typical multiplexer has n control inputs (S_{n-1}, \dots, S_0) called *selection inputs*, 2^n information inputs (I_{2^n-1}, \dots, I_0), and one output Y
- A multiplexer can be designed to have m information inputs with $m < 2^n$ as well as n selection inputs


2-to-1-Line Multiplexer

- Since $2 = 2^1$, $n = 1$
- The single selection variable S has two values:
 - ⑩ $S = 0$ selects input I_0
 - ⑩ $S = 1$ selects input I_1

- The equation:

$$Y = \bar{S}I_0 + SI_1$$

- The circuit:

 


2-to-1-Line Multiplexer (continued)


- **Note the regions of the multiplexer circuit shown:**
 - ⑩ 1-to-2-line Decoder
 - ⑩ 2 Enabling circuits
 - ⑩ 2-input OR gate
- **To obtain a basis for multiplexer expansion, we combine the Enabling circuits and OR gate into a 2×2 AND-OR circuit:**
 - ⑩ 1-to-2-line decoder
 - ⑩ 2×2 AND-OR
- **In general, for an 2^n -to-1-line multiplexer:**
 - ⑩ n -to- 2^n -line decoder
 - ⑩ $2^n \times 2$ AND-OR

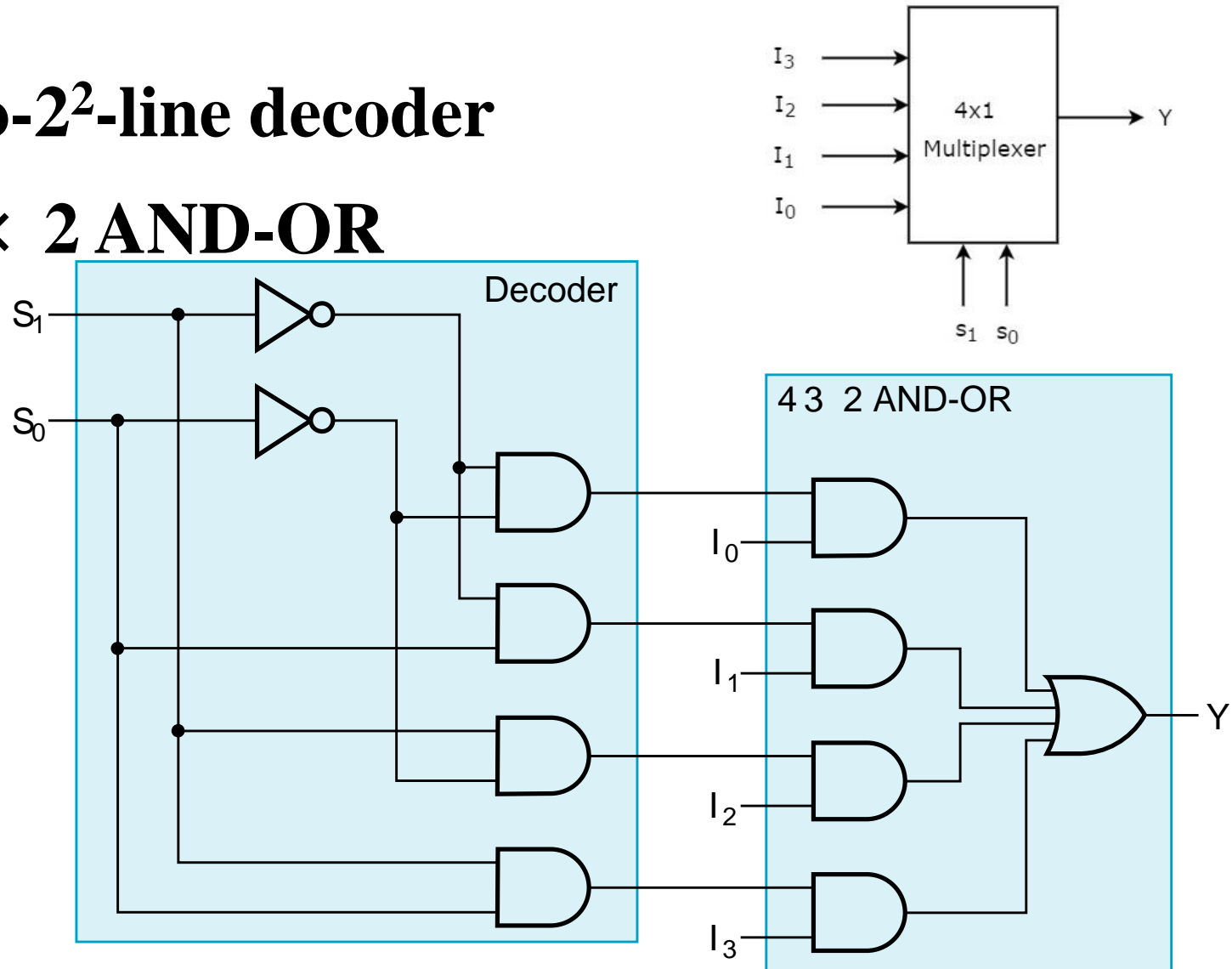Example: 4-to-1-line Multiplexer

- 2-to- 2^2 -line decoder
- $2^2 \times 2$ AND-OR




Example: 8-to-1-line Multiplexer

 


Select Data Inputs			Output
S ₂	S ₁	S ₀	Y
0	0	0	D ₀
0	0	1	D ₁
0	1	0	D ₂
0	1	1	D ₃
1	0	0	D ₄
1	0	1	D ₅
1	1	0	D ₆
1	1	1	D ₇

Example: 8-to-1-line Multiplexer

 


Multiplexer Expansion

- 8-to-1 MUX using Dual 4-to-1 MUX

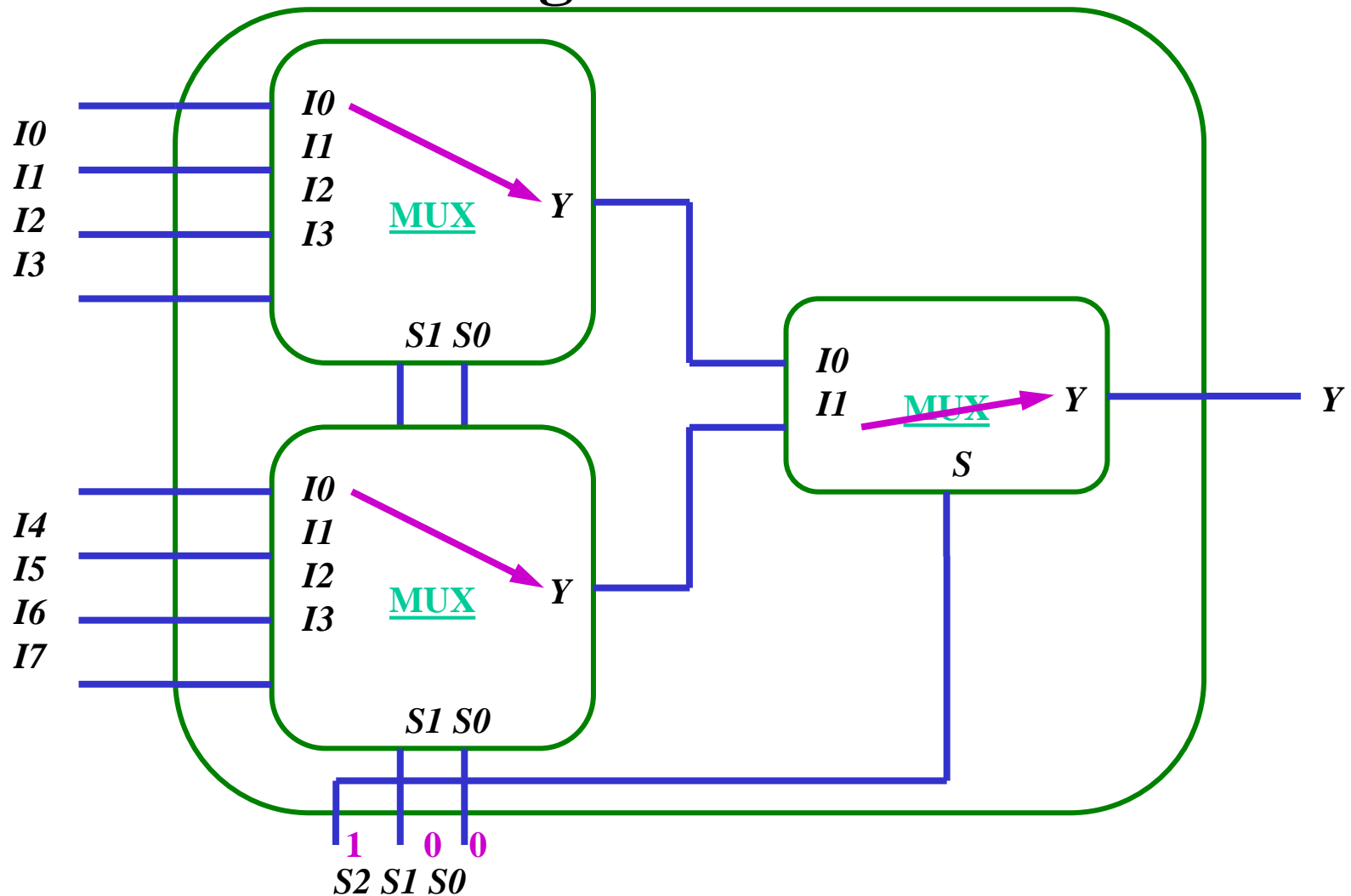

Multiplexer Width Expansion

 - Select “vectors of bits” instead of “bits”
- Use multiple copies of $2^n \times 2$ AND-OR in parallel
- Example:
4-to-1-line quad multi-plexer



Combinational Circuits using Multiplexer


Approach 1: Using n number of selection lines

Approach 2: Using $n-1$ number of selection lines

Implementation Using Multiplexers

★ Example

$$F(x, y) = \sum(0, 1, 3)$$

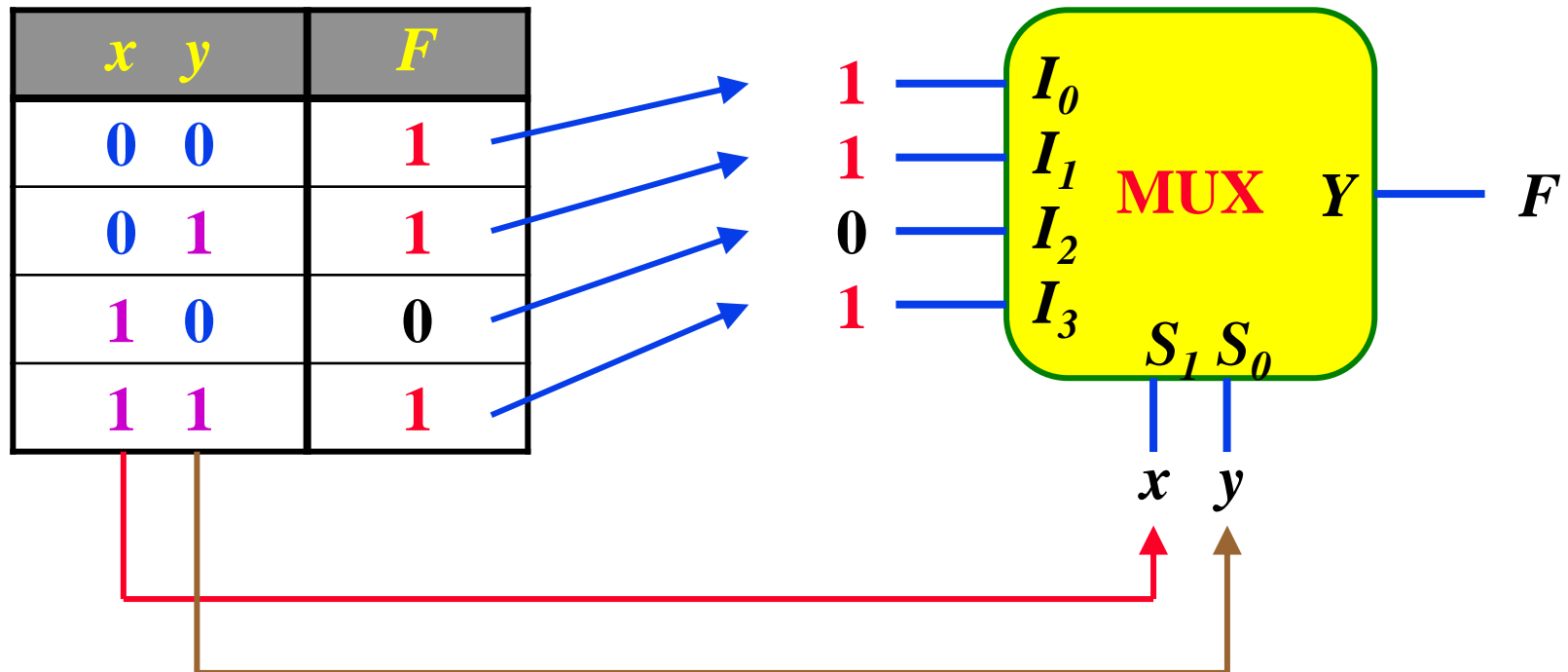


Implementation Using Multiplexers

★ Example

$$F(x, y, z) = \sum(1, 2, 6, 7)$$

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 

Implementation Using Multiplexers

★ Example

$$F(x, y, z) = \sum(1, 2, 6, 7)$$


x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$F = z$

$F = \bar{z}$

$F = 0$


$F = 1$

 




Implementation Using Multiplexers

★ Example
 
$$F(A, B, C, D) = \sum(1, 3, 4, 11, 12, 13, 14, 15)$$




DeMultiplexers

  
 


S_1	S_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	I
0	1	0	0	I	0
1	0	0	I	0	0
1	1	I	0	0	0


Multiplexer / DeMultiplexer Pairs

 

DeMultiplexers / Decoders

  

S_1	S_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	I
0	1	0	0	I	0
1	0	0	I	0	0
1	1	I	0	0	0

 

E	I_1	I_0	Y_3	Y_2	Y_1	Y_0
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0



Half Adder


- A half adder is an arithmetic circuit that generates the sum of two binary digits.
- The circuit has two inputs and two outputs.

Truth Table of Half Adder

Inputs		Outputs	
X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = \bar{X}Y + X\bar{Y} = X \oplus Y$$

$$C = XY$$

 

Full Adder

- A full adder is a combinational circuit that forms the arithmetic sum of three input bits.
- Besides the three inputs, it has two outputs.

Truth Table of Full Adder

Inputs			Outputs	
X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = \overline{X}\overline{Y}Z + \overline{X}Y\overline{Z} + X\overline{Y}\overline{Z} + XYZ$$

$$C = XY + XZ + YZ$$

K-map: For sum

		Y			
		YZ		11	10
X	0	00	01	11	10
	1	00	01	11	10
		Z			

$$S = \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XYZ$$

$$= \bar{X}(\bar{Y}Z + Y\bar{Z}) + X(\bar{Y}\bar{Z} + YZ)$$

$$= \bar{X}(Y \oplus Z) + X(Y \odot Z)$$


$$\text{Let's say } Y \oplus Z = A, Y \odot Z = \bar{A}$$

$$= \bar{X}A + X\bar{A}$$

$$= X \oplus A$$

$$= X \oplus Y \oplus Z$$

K-map: For Carry

 

$$\begin{aligned}
 C &= XY + XZ + YZ \\
 &= XY + Z(X\bar{Y} + \bar{X}Y) \\
 &= XY + Z(X \oplus Y)
 \end{aligned}$$

$$\begin{aligned}
 C &= XY + XZ + YZ \\
 &= XY + XZ + YZ (X + X') \\
 &= XYZ + XY + XZ + X'YZ \\
 &= XY(Z+1) + XZ + X'YZ \\
 &= XY + XZ + X'YZ \\
 &= XY + XZ (Y + Y') + X'YZ \\
 &= XY + XYZ + XY'Z + X'YZ \\
 &= XY (1+Z) + XY'Z + X'YZ \\
 &= XY + XY'Z + X'YZ \\
 &= XY + Z (XY' + X'Y) \\
 &= XY + Z (X \oplus Y)
 \end{aligned}$$