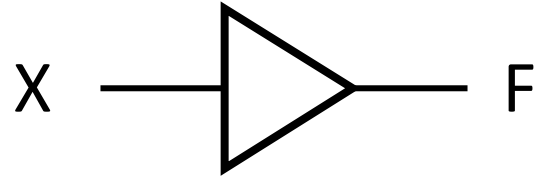


Digital Logic Design

Lecture 13

Buffer

- A buffer is a gate with the function $F = X$:



- In terms of Boolean function, a buffer is the same as a connection!
- So why use it?
 - A buffer is an electronic amplifier used to improve circuit voltage levels and increase the speed of circuit operation.

Design a circuit that accepts 3-bit number and generates a 6 bit binary number equal to square of the given number

A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

S5	S4	S3	S2	S1	S0
0	0	0	0	0	0
0	0	0	0	0	1
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	0	0
0	1	1	0	0	1
1	0	0	1	0	0
1	↓	0	0	0	1

K-map for S0:

A \ BC

0	1	1	0
0	1	1	0

$$S0 = C$$

K-map for S2:

A \ BC				
	00	01	10	11
0	0	0	0	1
1	0	0	0	1

$$S2 = BC'$$

K-map for S3:

A \ BC				
	00	01	10	11
0	0	0	1	0
1	0	1	0	0

$$S3 = AB'C + A'BC$$

K-map for S4:

A \ BC				
	00	01	10	11
0	0	0	0	0
1	1	1	1	0

$$S4 = AB' + AC$$

K-map for S5:

A \ BC				
	00	01	10	11
0	0	0	0	0
1	0	0	1	1


$$S5 = AB$$

Analysis Procedure

- The design of a combinational circuit starts from the verbal specifications of a required function and ends with a set of output Boolean functions or a logic diagram.
- The analysis of a combinational circuit is somewhat the reverse process.
- It starts with a given logic diagram and ends with a set of Boolean functions, a truth table or a verbal explanation of the circuit operation.

Analysis Procedure

- Boolean Expression Approach

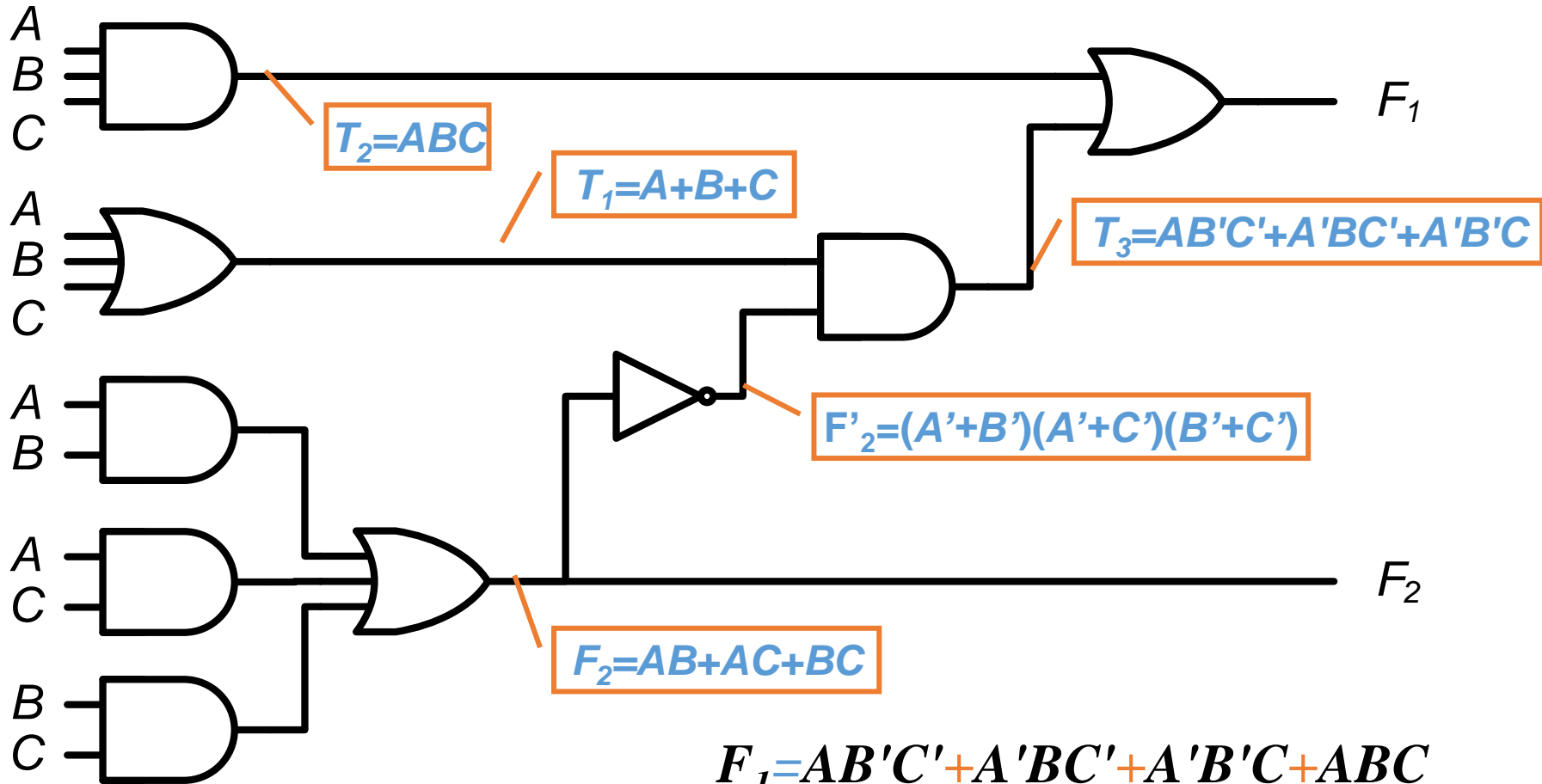


$$F_1 = AB'C' + A'BC' + A'B'C + ABC$$

$$F_2 = AB + AC + BC$$


Analysis Procedure

- **Truth Table Approach**

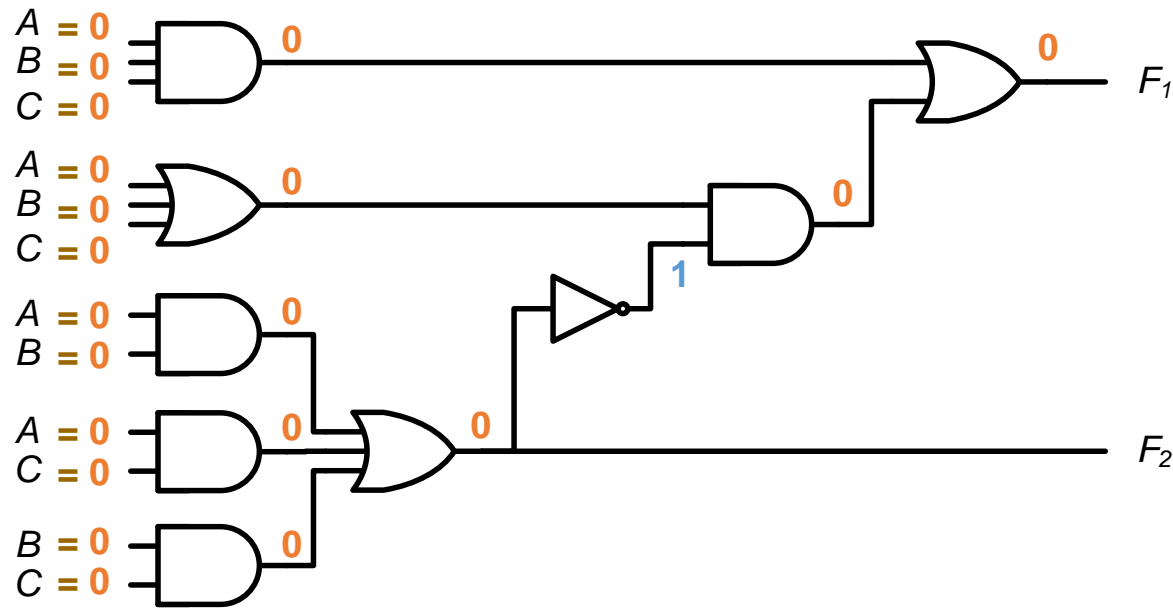[illegible]


Analysis Procedure

- **Truth Table Approach**

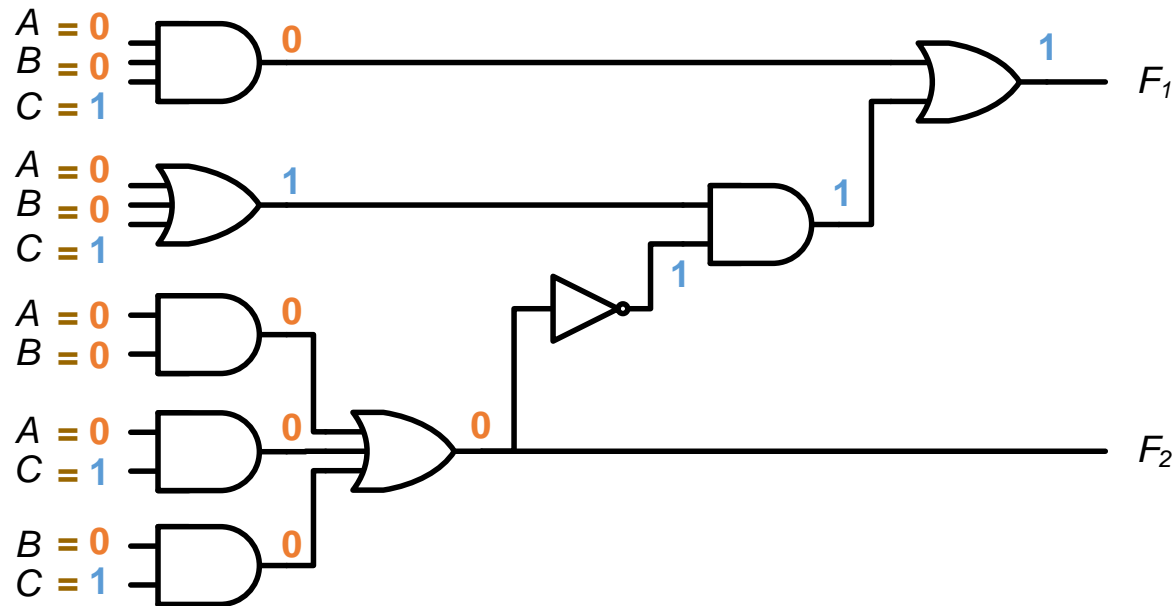[illegible]

Analysis Procedure


- Truth Table Approach

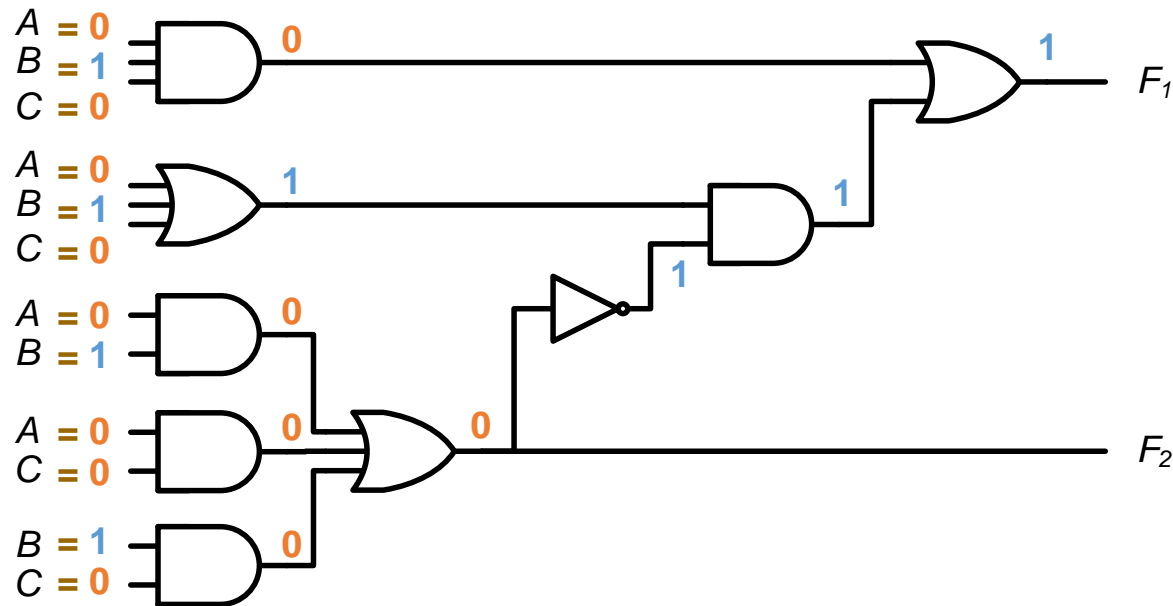

A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0

Analysis Procedure


- Truth Table Approach

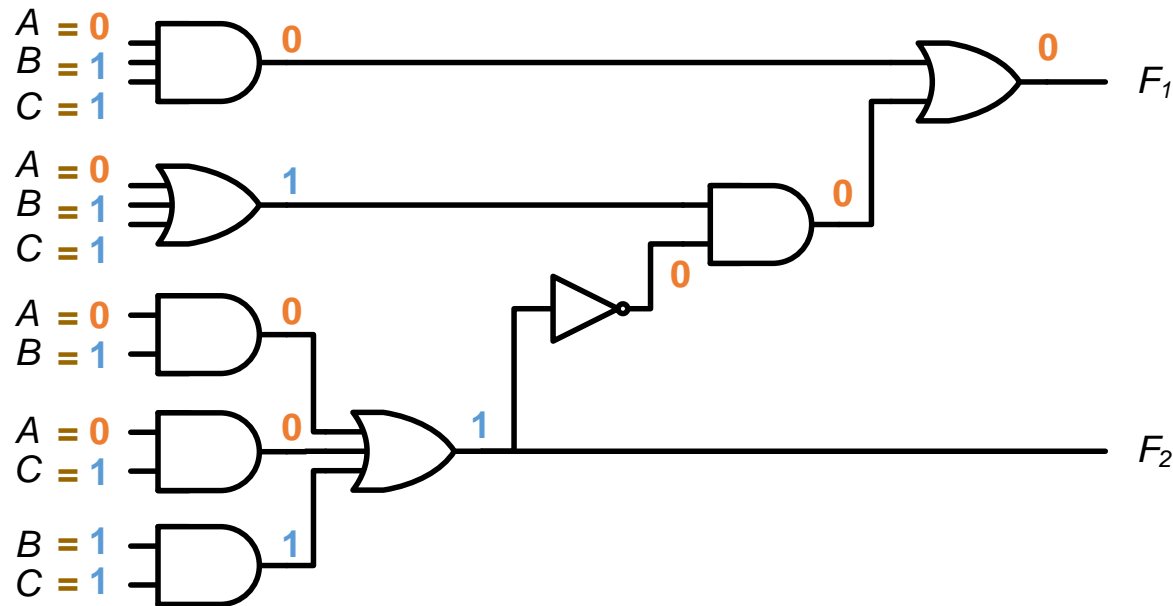

A	B	C	F ₁	F ₂
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1

Analysis Procedure


- Truth Table Approach

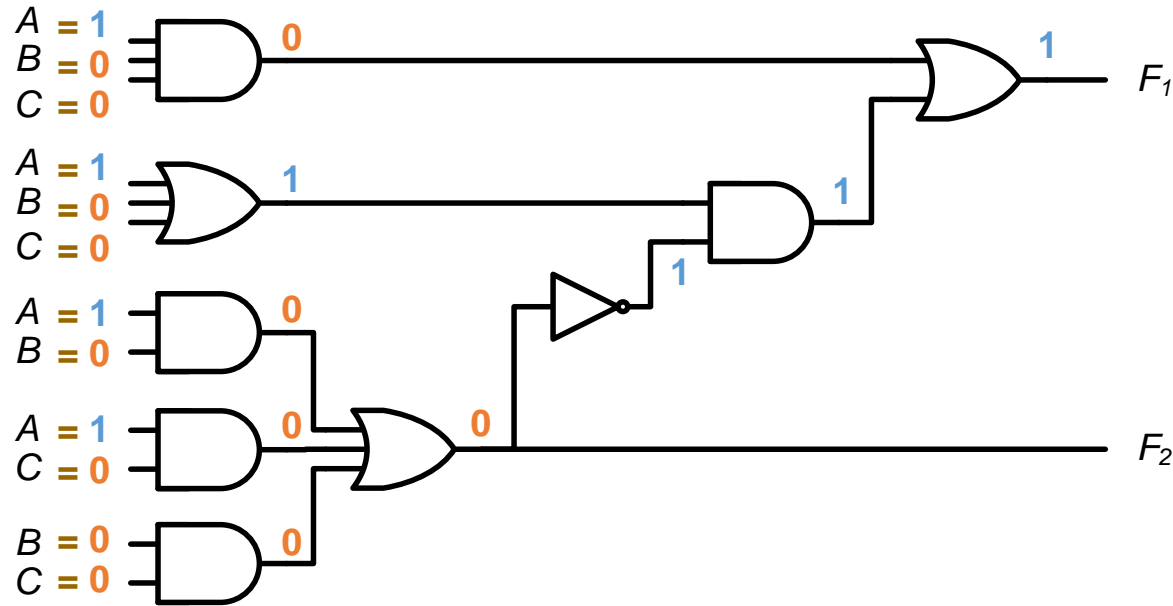

A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0

Analysis Procedure


- Truth Table Approach

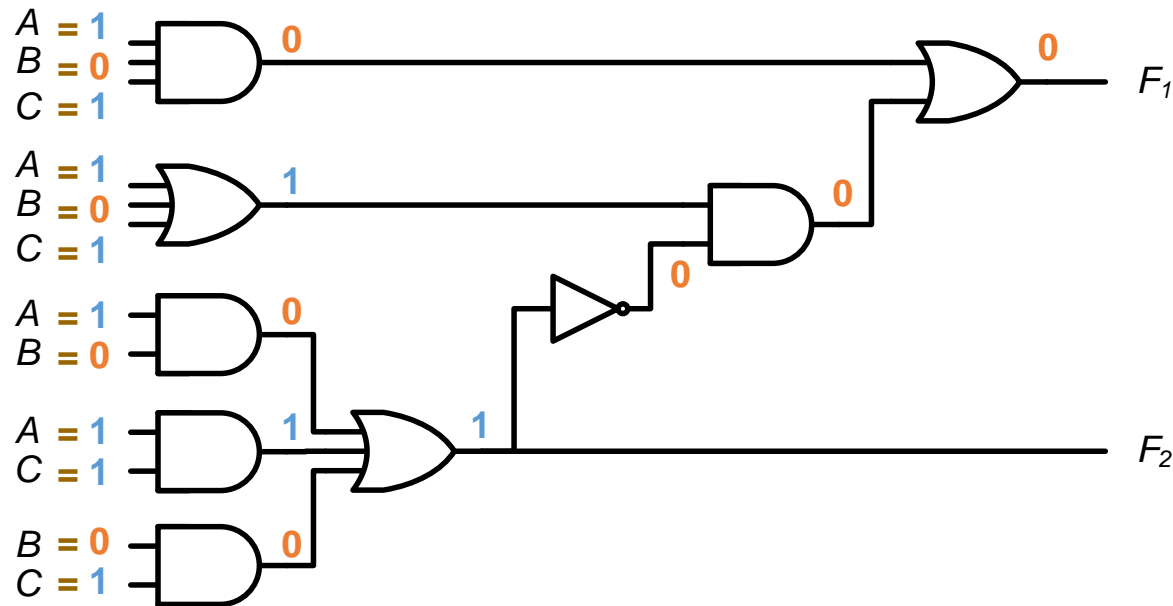

A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1

Analysis Procedure


- Truth Table Approach

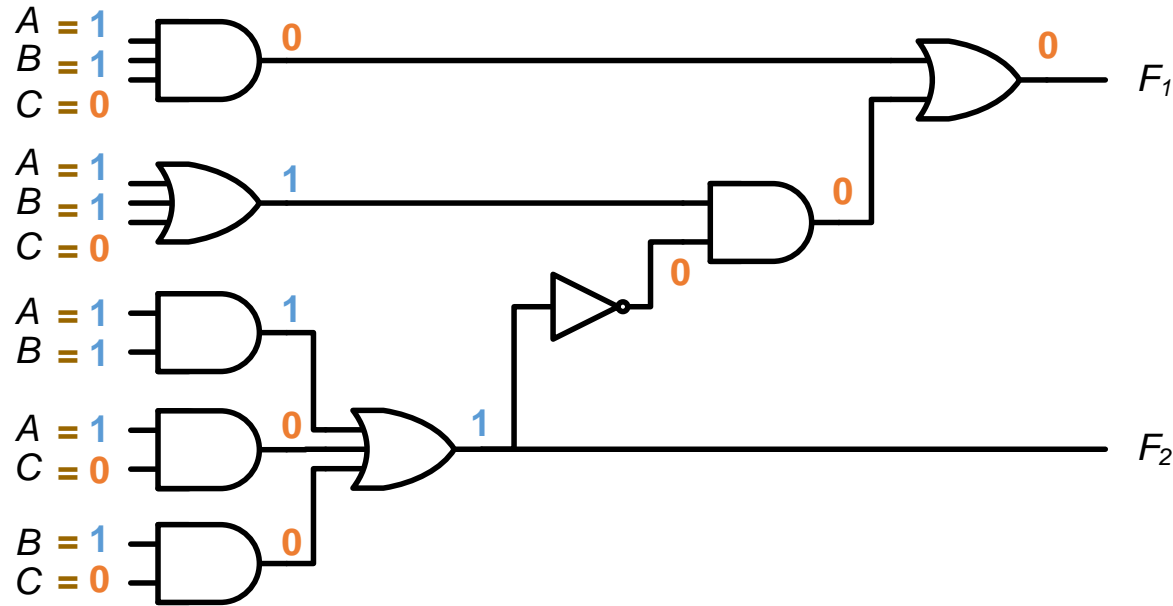

A	B	C	F ₁	F ₂
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1

Analysis Procedure

- Truth Table Approach

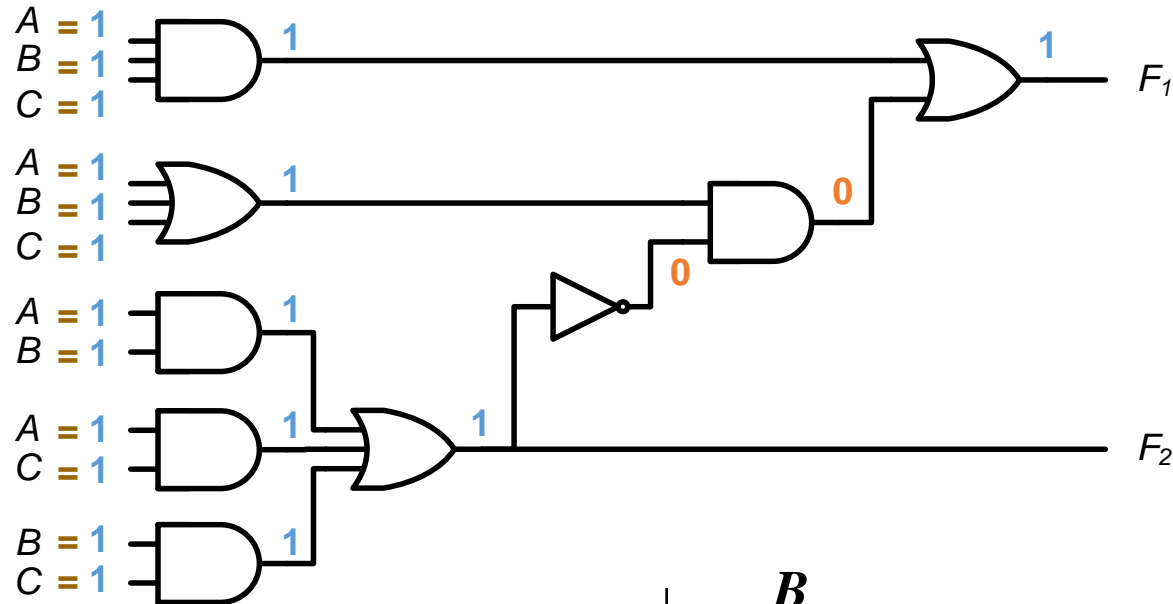

A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

	B			
	0	1	0	1
A	1	0	1	0
	C			

	B			
	0	0	1	0
A	0	1	1	1
	C			

$$F_1 = AB'C' + A'BC' + A'B'C + ABC$$

$$F_2 = AB + AC + BC$$

Code Converter

- The availability of a large variety of codes for the same discrete elements of information results in the use of different codes by different digital systems.
- It is sometimes necessary to use the output of one system as the input to another.
- A code conversion circuit must be inserted between the two systems if each uses different codes for the same information.
- Thus, a code converter is a circuit that makes the two systems compatible even though each uses a different binary code.

Contd.

- To convert from binary code A to binary code B, the input lines must supply the bit combination of elements as specified by code A and the output line must generate the corresponding bit combination of code B.
- A combinational circuit perform this transformation by means of logic gates.
- The design procedure of code converters will be illustrated by means of a specific example of conversion from the BCD to the excess-3 code.


Design Procedure:

Given a problem statement:

- Determine the number of *inputs* and *outputs*
- Derive the truth table
- Simplify the Boolean expression for each output
- Produce the required circuit




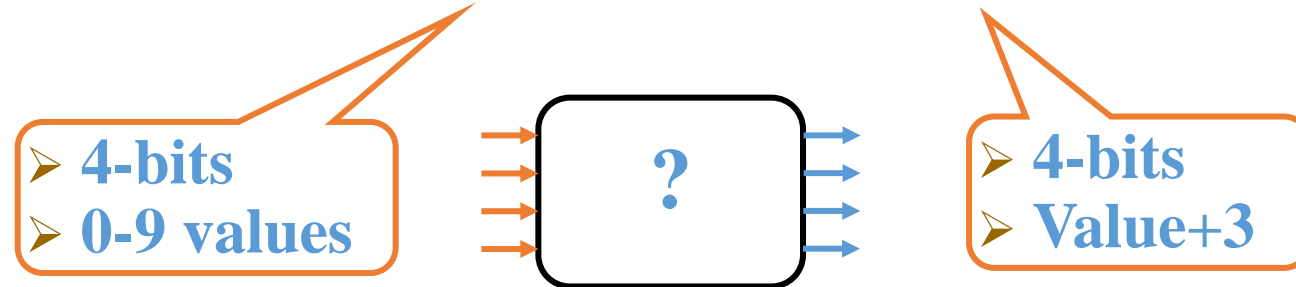
Example:

Design a circuit to convert a “BCD” code to “Excess 3” code




BCD-to-Excess 3 Converter

<i>A B C D</i>	<i>w x y z</i>
0 0 0 0	0 0 1 1
0 0 0 1	0 1 0 0
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 0
0 1 0 0	0 1 1 1
0 1 0 1	1 0 0 0
0 1 1 0	1 0 0 1
0 1 1 1	1 0 1 0
1 0 0 0	1 0 1 1
1 0 0 1	1 1 0 0
1 0 1 0	x x x x
1 0 1 1	x x x x
1 1 0 0	x x x x
1 1 0 1	x x x x
1 1 1 0	x x x x
1 1 1 1	x x x x

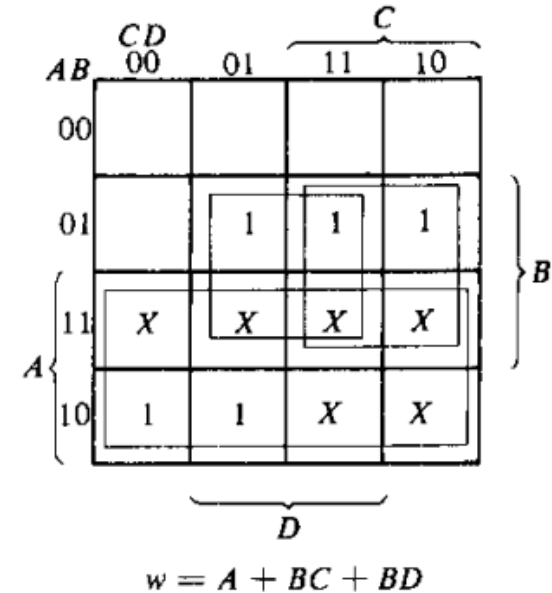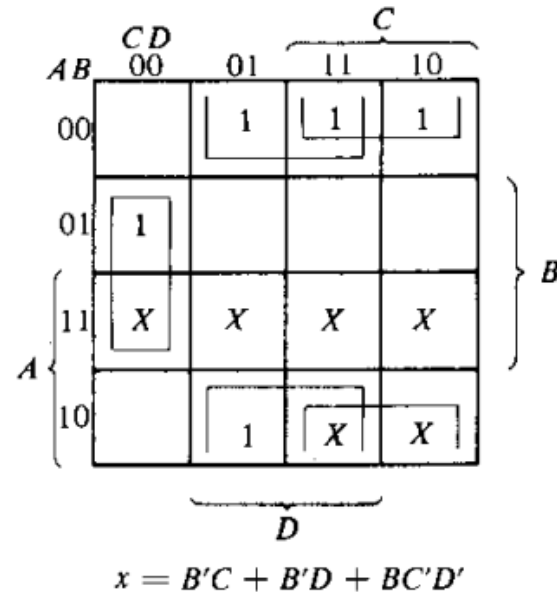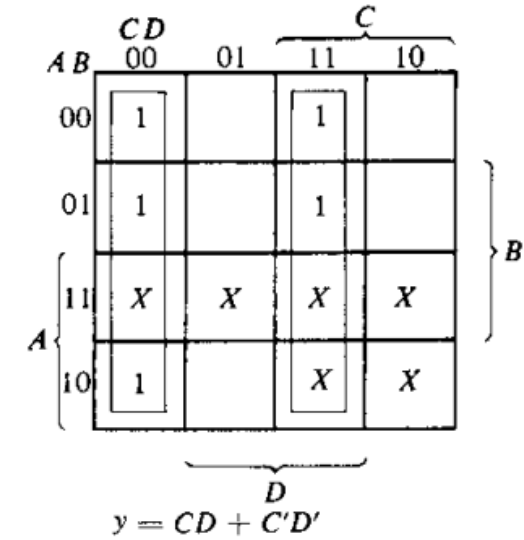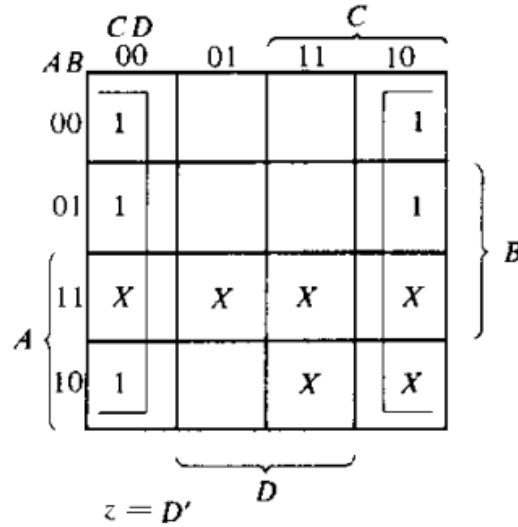

BCD-to-Excess 3 Converter

<i>A B C D</i>	<i>w x y z</i>
0 0 0 0	0 0 1 1
0 0 0 1	0 1 0 0
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 0
0 1 0 0	0 1 1 1
0 1 0 1	1 0 0 0
0 1 1 0	1 0 0 1
0 1 1 1	1 0 1 0
1 0 0 0	1 0 1 1
1 0 0 1	1 1 0 0
1 0 1 0	x x x x
1 0 1 1	x x x x
1 1 0 0	x x x x
1 1 0 1	x x x x
1 1 1 0	x x x x
1 1 1 1	x x x x

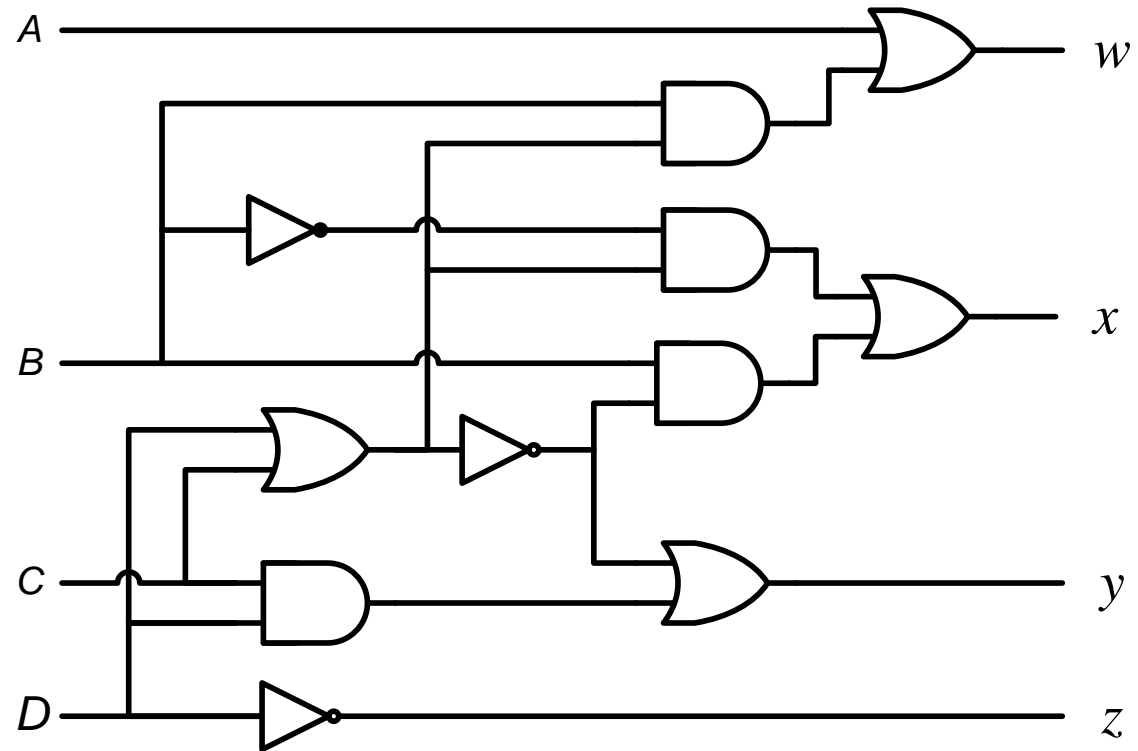

$$w = A + B(C+D)$$

$$y = (C+D)' + CD$$

$$x = B'(C+D) + B(C+D)'$$

$$z = D'$$

Gray to Binary Code

- Design a circuit to convert a 3-bit Gray code to a binary code
- The formulation gives the truth table on the right
- It is obvious from this table that $X = A$ and the Y and Z are more complex

Gray A B C	Binary X Y Z
0 0 0	0 0 0
0 0 1	0 0 1
0 1 1	0 1 0
0 1 0	0 1 1
1 1 0	1 0 0
1 1 1	1 0 1
1 0 1	1 1 0
1 0 0	1 1 1

Seven-Segment Decoder

- A **digital or binary decoder** is a digital combinational logic circuit which can convert one form of digital code into another form.
- **BCD to 7-segment** display decoder is a special decoder which can convert binary coded decimals into another form which can be easily displayed through a 7-segment display.

BCD




- **BCD stands for binary coded decimal.**
- **It is a digital numbering system in which we can represent each decimal number using 4 bits of binary numbers.**
- **There are 10 digits in the decimal system. To represent all 10 digits we need 10 combinations of 4 binary bits.**

7-Segment Display

- It is a digital device that can be used for displaying decimal number, alphabets, and characters.
- 7-Segment display contains 7 LED segments arranged in a shape given in figure.
- Generally, there are 8 input pins in a 7-Segment display.
- 7 input pins for each of the 7 LEDs and one pin for the common terminal.

Seven-Segment Decoder

<i>w x y z</i>	<i>a b c d e f g</i>
0 0 0 0	1 1 1 1 1 1 0
0 0 0 1	0 1 1 0 0 0 0
0 0 1 0	1 1 0 1 1 0 1
0 0 1 1	1 1 1 1 0 0 1
0 1 0 0	0 1 1 0 0 1 1
0 1 0 1	1 0 1 1 0 1 1
0 1 1 0	1 0 1 1 1 1 1
0 1 1 1	1 1 1 0 0 0 0
1 0 0 0	1 1 1 1 1 1 1
1 0 0 1	1 1 1 1 0 1 1
1 0 1 0	x x x x x x x
1 0 1 1	x x x x x x x
1 1 0 0	x x x x x x x
1 1 0 1	x x x x x x x
1 1 1 0	x x x x x x x
1 1 1 1	x x x x x x x

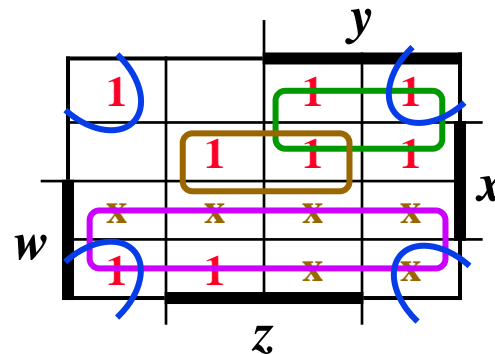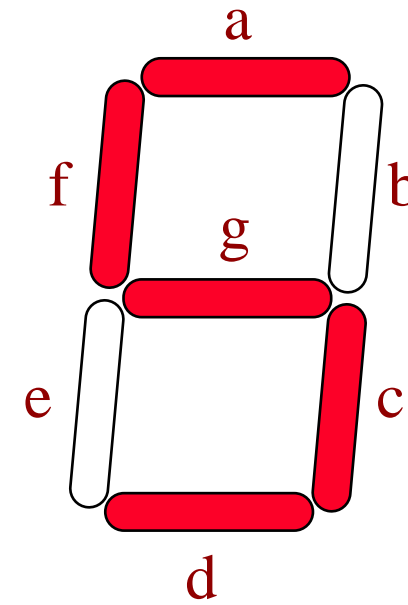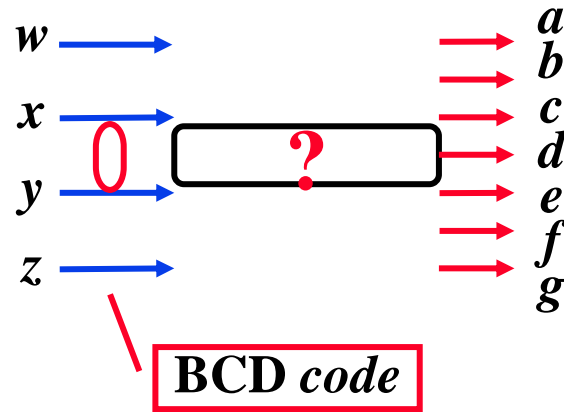

$$a = w + y + xz + x'z'$$

$$b = \dots$$

$$c = \dots$$

$$d = \dots$$

Why we need this decoder?

- **A digital system like a computer can understand and easily read a large number in binary format.**
- **However, a human cannot read large binary numbers.**
- **To solve this problem we need to display it as a decimal digit using 7-segment display.**